


Kevan Haghshenas  
Digital Logic Design

September 20, 2017  
HW 2:

HW2: 11-15, 21, 40-41, 59-62, 78

1) Function Table:


A	B	C	D	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	$Q_7$	$Q_8$	Z	
L	L	L	L	off	on	off	on	off	on	off	on	off	H
L	L	L	H	off	on	off	on	on	on	off	off	off	L
L	L	H	L	off	on	off	on	off	off	on	on	on	L
L	L	H	H	off	on	off	on	on	off	on	on	off	L
L	H	L	L	off	on	on	off	off	off	on	off	on	H
L	H	L	H	off	on	on	off	off	on	on	off	off	L
L	H	H	L	off	on	on	off	off	off	off	on	on	L
L	H	H	H	off	on	on	off	off	on	off	on	off	L
H	L	L	L	on	off	off	on	off	on	on	off	on	H
H	L	L	H	on	off	off	on	on	off	on	off	off	L
H	L	H	L	on	off	off	on	off	off	on	on	on	L
H	H	L	H	on	off	off	on	off	off	on	off	on	L
H	H	H	L	on	off	off	on	off	off	on	off	off	L
H	H	H	H	on	off	off	on	off	off	on	on	on	L

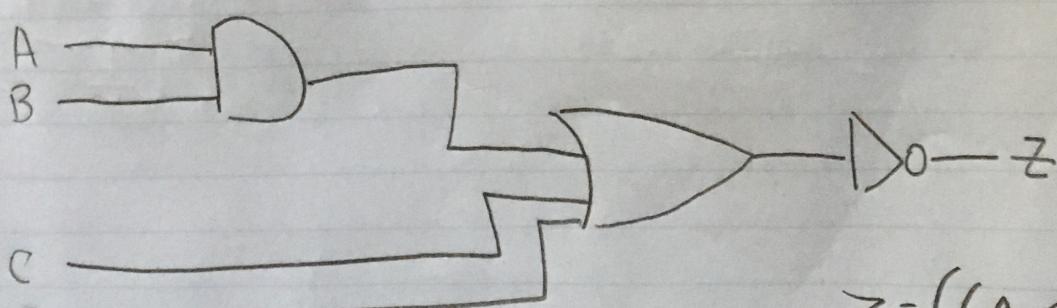

$$Z = ((A \cdot B) + (C + D))$$

12)



A	B	C	D	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	$Q_7$	$Q_8$	Z
L	L	L	0	1	0	1	0	1	0	0	1	H
L	L	L	H	0	1	0	1	0	1	0	0	H
L	L	L	L	0	1	0	1	1	0	0	1	H
L	L	L	H	0	1	0	1	1	0	1	0	H
L	H	L	L	0	1	1	0	0	1	0	1	H
L	H	L	H	0	1	1	0	0	1	0	0	H
L	H	H	L	0	1	1	0	1	0	0	1	H
L	H	H	H	0	1	1	0	1	0	1	0	L
H	L	L	L	1	0	0	1	0	1	0	1	H
H	L	L	H	1	0	0	1	0	1	0	0	H
H	L	H	L	1	0	0	1	1	0	0	1	H
H	H	L	L	1	0	1	0	0	1	0	1	L
H	H	L	H	1	0	1	0	0	1	1	0	H
H	H	H	L	1	0	1	0	1	0	0	1	H
H	H	H	H	1	0	1	0	1	0	1	0	L

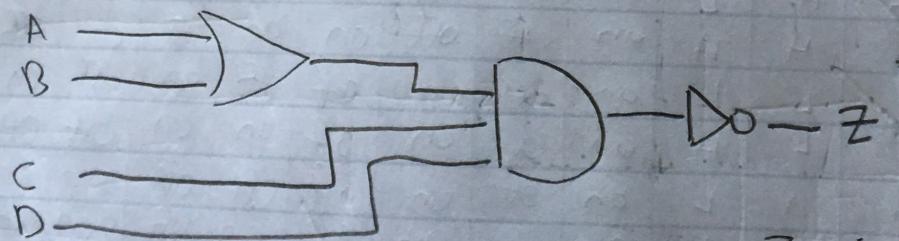

$$Z = ((A+B) \cdot C \cdot D)$$




13)

A	B	C	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	Z
L	L	L	0	1	G	1	0	1	H
L	L	H	0	1	G	1	1	0	L
L	H	L	0	1	1	0	0	1	L
L	H	H	0	1	1	0	1	0	L
U	L	L	1	0	G	1	0	1	L
H	L	A	1	0	G	1	1	0	L
H	H	L	1	6	1	0	G	1	L
H	H	H	1	6	1	G	1	0	L

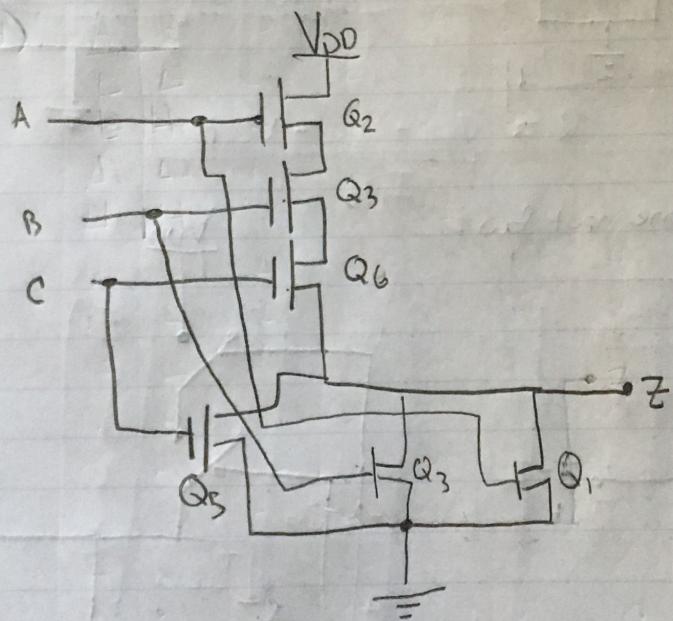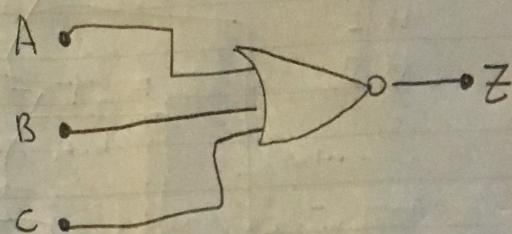


14)  $A|B$


L	L
L	H
H	L
H	H

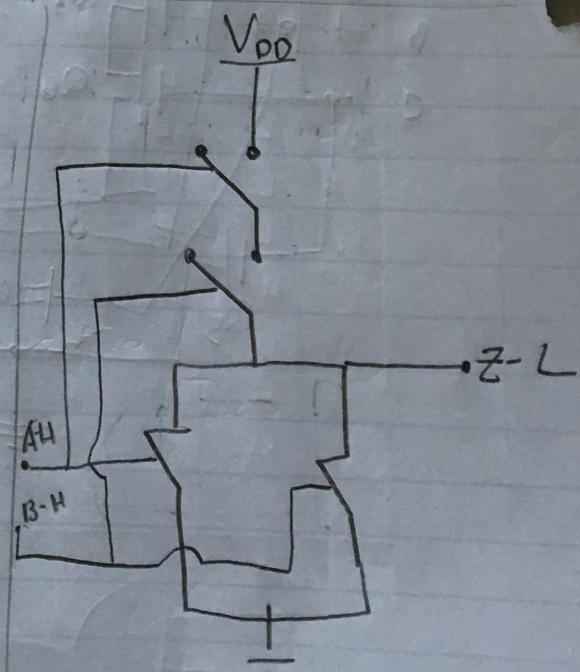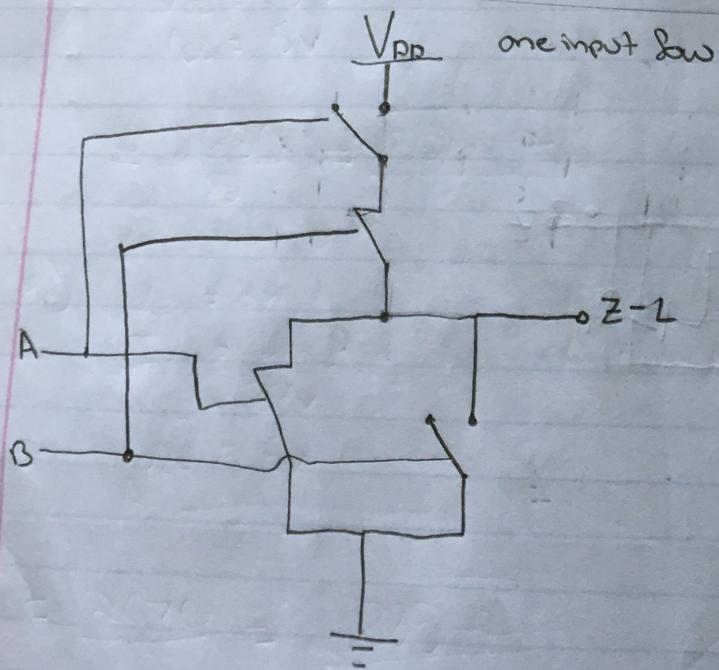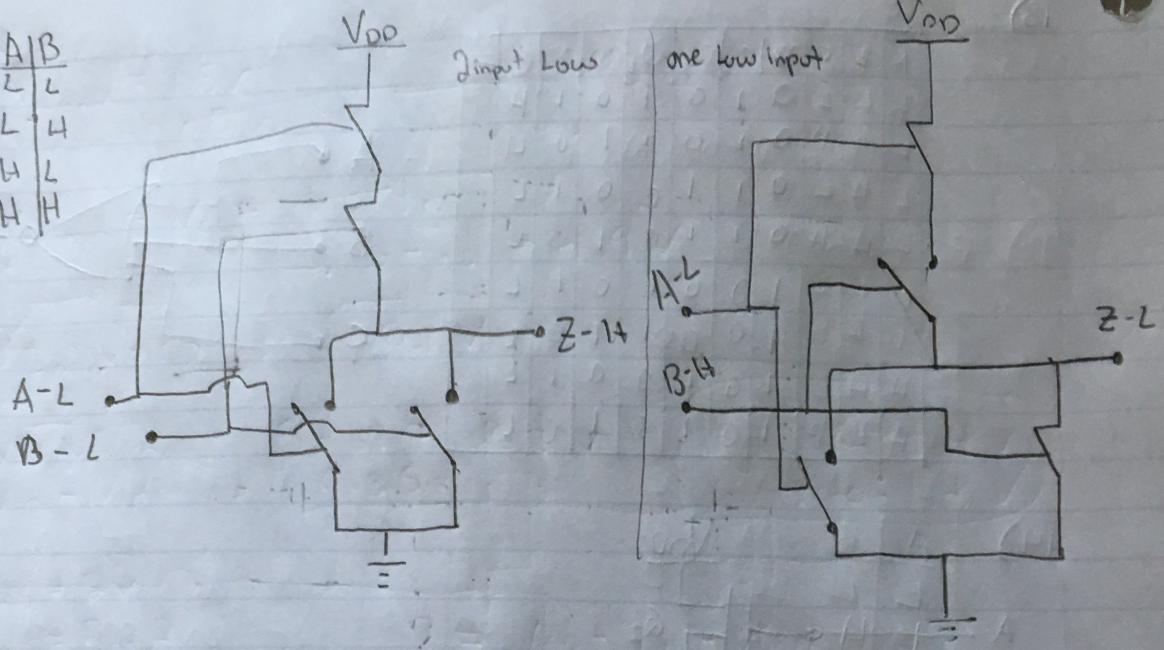

15)

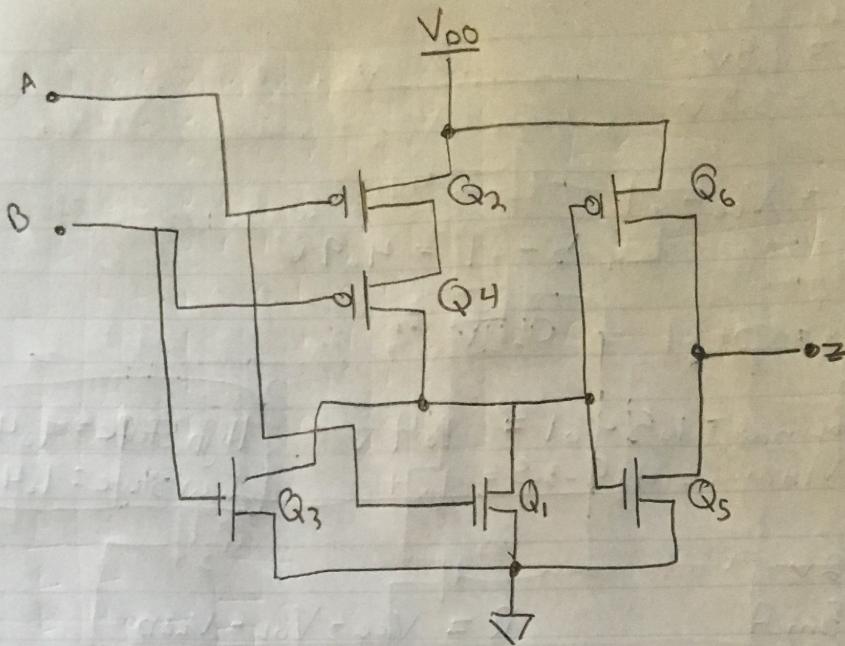

A	B	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub>	Q <sub>5</sub>	Q <sub>6</sub>	Z
L	L	G	1	0	1	0	0	L
L	H	O	1	1	0	0	1	H
H	L	I	0	0	1	0	1	H
H	H	A	1	0	1	0	1	H

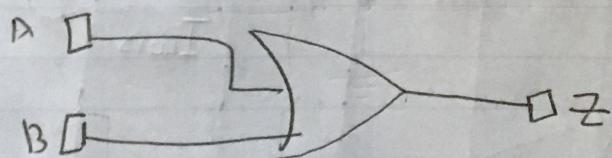

21.

$$V_{IL\max} = 1.5V$$

$$V_{IH\min} = 3.5V$$

$$V_{O\min} = V_{CC} - 0.1 \rightarrow 5 - 0.1 = 4.9V$$

$$V_{O\max} = 0 + 0.1 = 0.1V$$

$$V_{IL\max} - V_{O\max} = 1.5 - 0.1 = 1.4V$$

$$V_{IH\min} - V_{O\min} = 3.5 - 4.9 = -1.4V$$

High State = 1.4V

Low State = 1.4V

40)  $V_{LED} = 2V$

$I_{LED} = 5mA$

$V_{OL} = 0.37$

$V_{CC} = 5V$

$$R = \frac{V_{CC} - V_{OL} - V_{LED}}{I_{LED}}$$

$$= \frac{2630}{5} = \boxed{526\Omega}$$

41)  $V_{LED} = 2V$

$I_{LED} = 2mA$


$V_{OL} = 0.33V$

$V_{CC} = 5V$


$$R = \frac{V_{CC} - V_{OL} - V_{LED}}{I_{LED}}$$

$$= \frac{2670}{2} = \boxed{1335\Omega}$$

$$59) Z = [A' + (B+C)]'$$

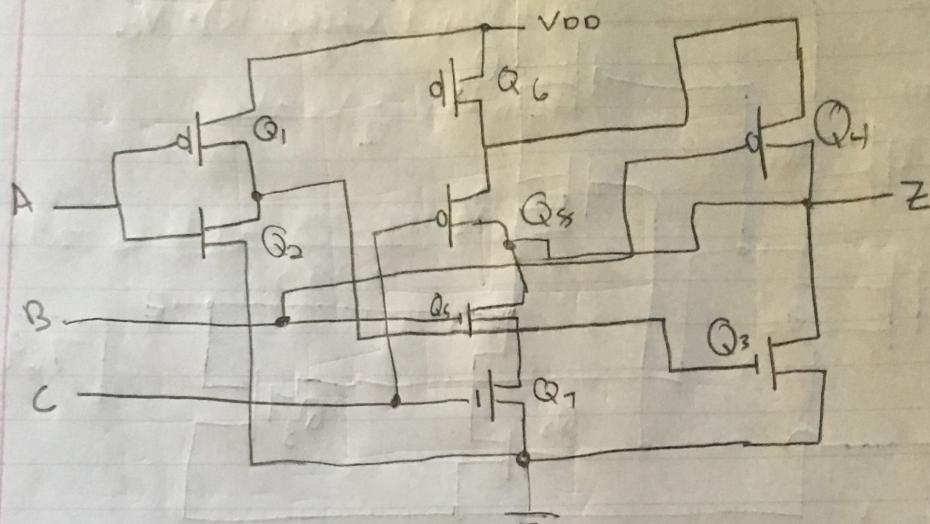


$$60) Z = [A' \cdot (B+C)]'$$

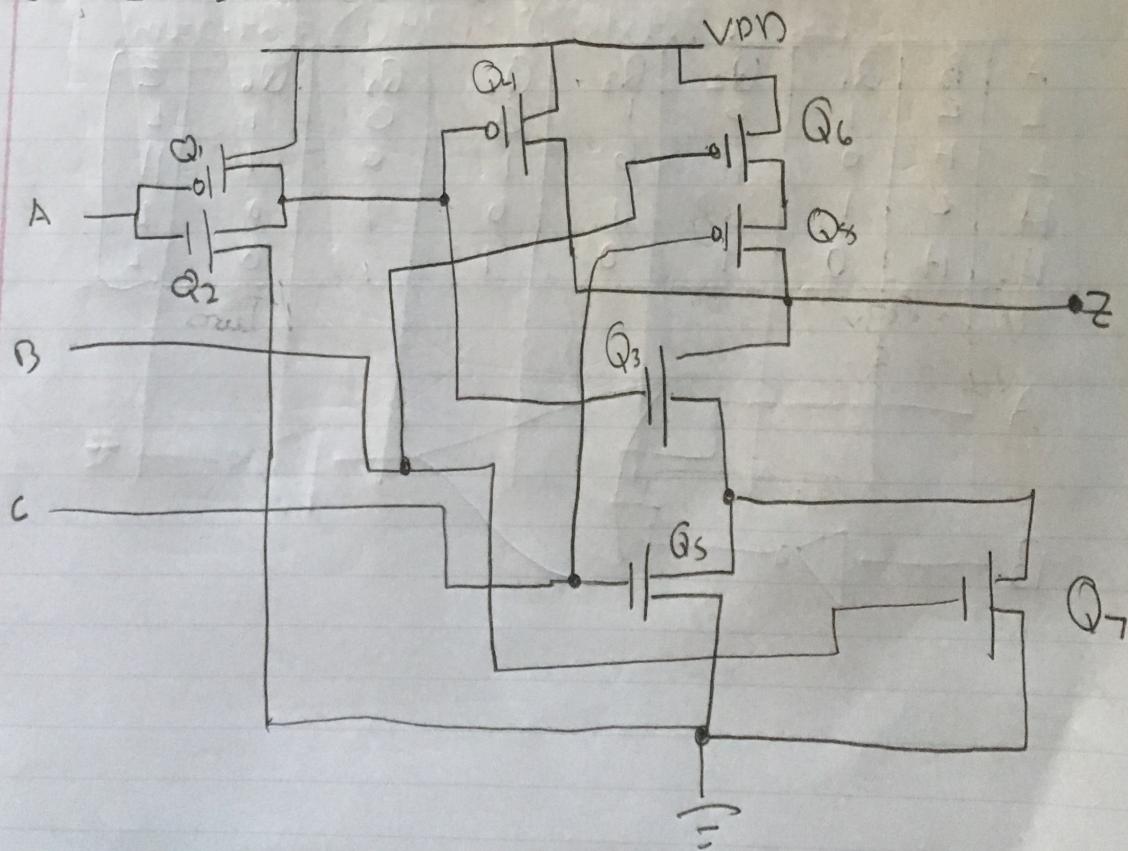

$$G) Z = (A+B')$$


$$(B \cdot A) + A' = AB$$

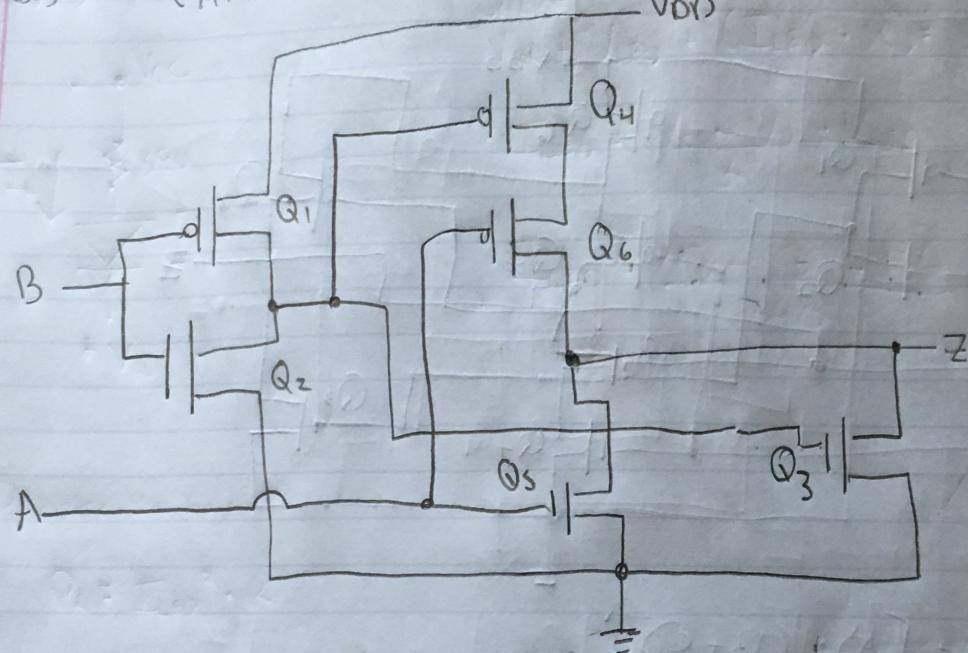


A	B	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	Z
L	L	1	0	1	0	1	0	L
L	H	0	1	0	1	0	1	H
H	L	1	0	1	0	1	0	L
H	H	0	1	0	1	1	0	L




$$G2) Z = (AB')$$

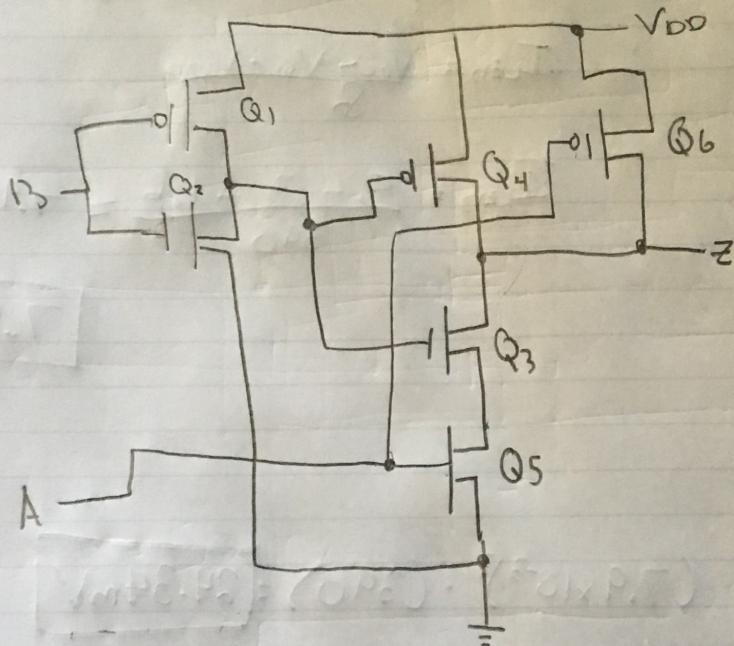

$A$	$B$	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$	$Q_6$	$Z$
L	L	1	0	1	0	1	0	H
L	H	0	1	0	1	0	1	H
H	L	1	0	1	0	1	0	L
H	H	0	1	0	1	1	0	H

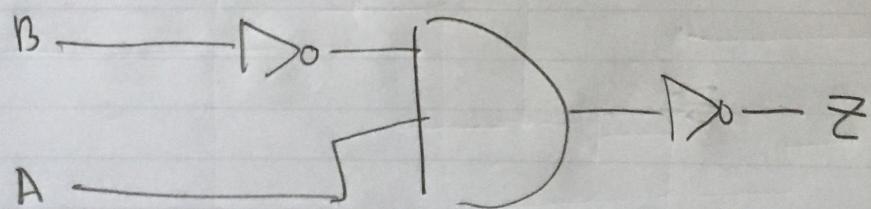

79)

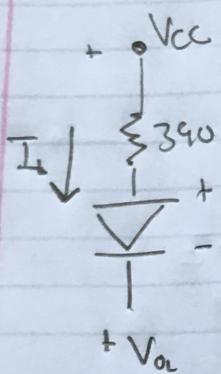

Current:

$$V_{OL} + V_{LED} + (I_{LED} \cdot R) = V_{CC}$$

$$I_{LED} = \frac{V_{CC} - V_{OL} - V_{LED}}{R}$$

$$I_{LED} = \frac{5 - 3 - 1.6}{390} = 7.9 \times 10^{-3}$$

7.9mA

Power:

$$P_L = I_{LED}^2 \cdot R$$

$$\hookrightarrow (7.9 \times 10^{-3})^2 \cdot (390) = \boxed{24.34 \text{ mW}}$$